



Electrical Engineering Department

Circuit analysis

Pspice assignment

Student name: Amal Ziad AbuHmoud

Student ID:1192141

Instructor: Wasel Ghanem

Date: 2/9/2021

Question 1:

For the circuit shown below, use Pspice to find V_o and the power absorbed/delivered by the 0.125Ω resistor and VCVS $2V_o$

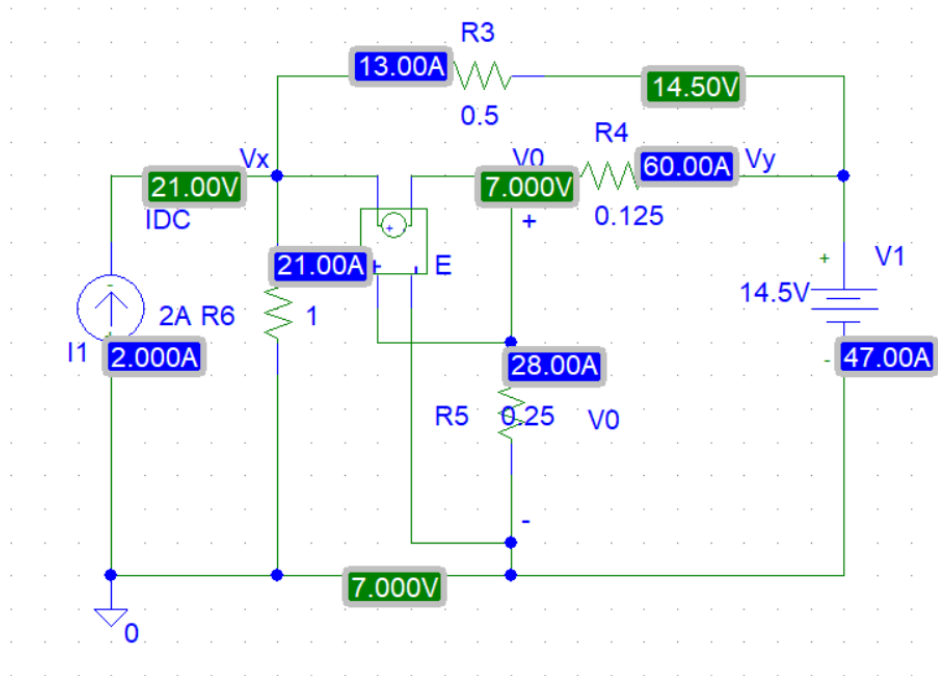


Fig.1.1

As shown in the figure 1.1:

$$V_0 = 7V$$

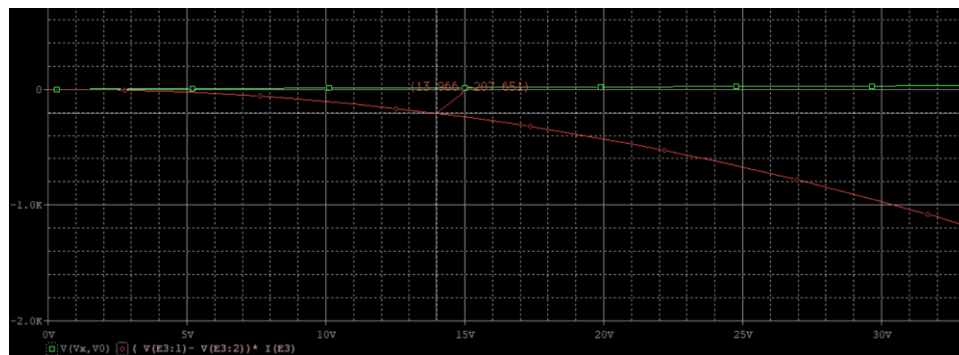


Fig1.2.1

As shown in fig.1.2.1 and its representation in fig.1.2.1:

We need power at $2V_0=14v$

So $P(\text{at } 2v_0)=-208 \text{ W}$ (delevired)

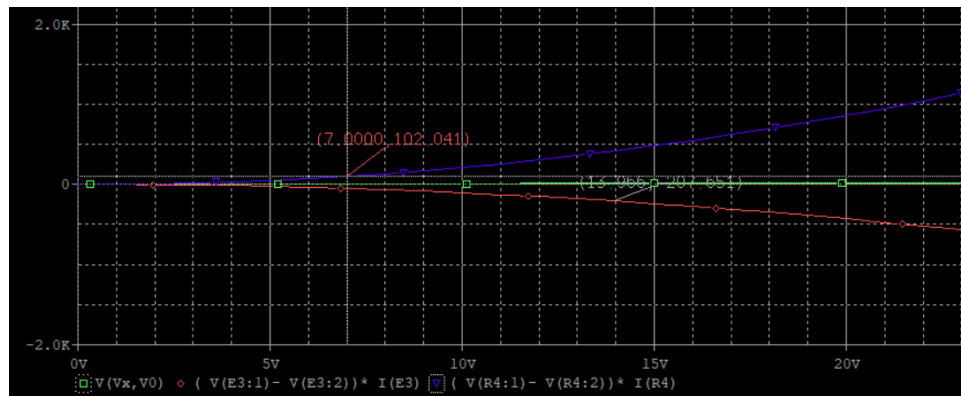


Fig.1.2.2

P at $R=0.125$, $P=102 \text{ W}$ (absorbed)

Question 2:

Determine the steady state voltage $v_o(t)$ for the circuit shown below using Pspice :

$$20\cos(5t)=20\sin(5t-\pi/2)$$

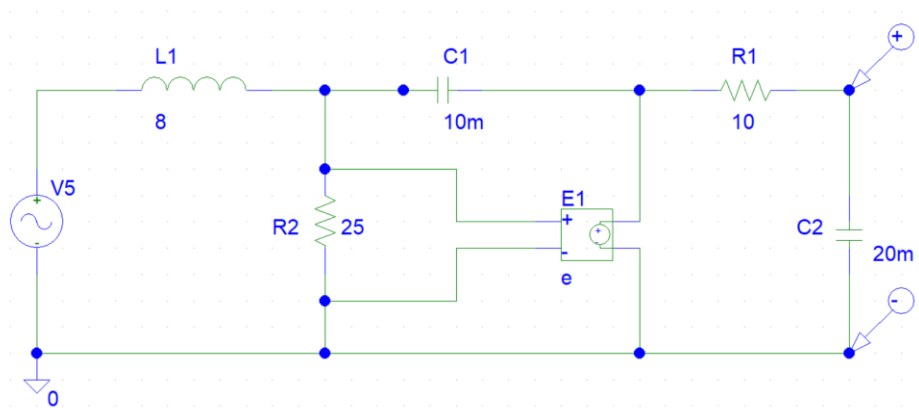


Fig.2.1

As shown in fig.2.1, after simulating it at transient we get:

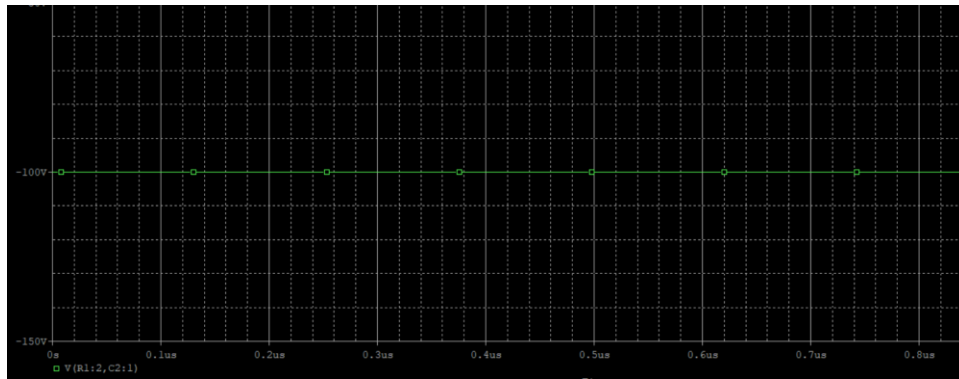


Fig.2.2

As shown in fig.2.2 the voltage $v_0(t) = -100V$

Question 3:

- Using Pspice, determine: the current $i_L(t)$ for $t > 0$ for the circuit in fig.3.1

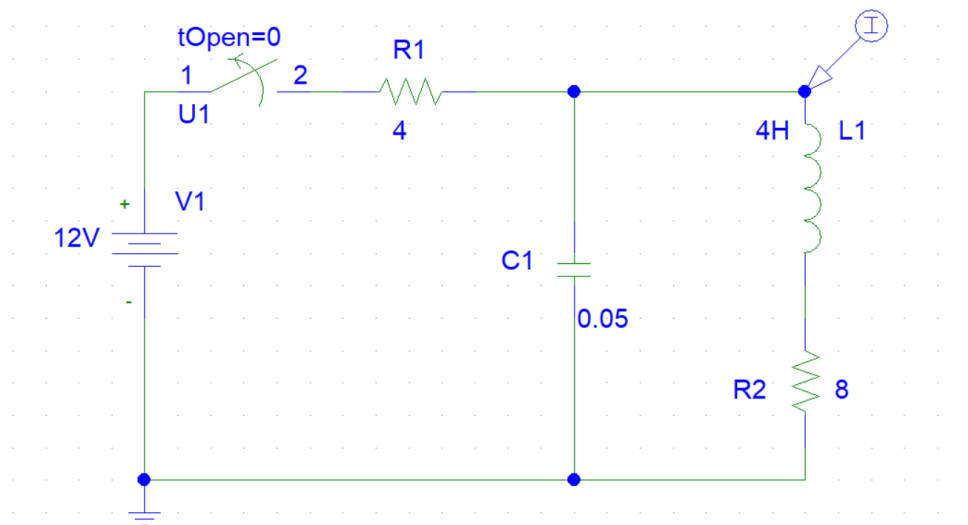


Fig.3.1.1

As shown in fig.3.1 we can find $i_L(t)$ for $t > 0$ by turning on bias current display:

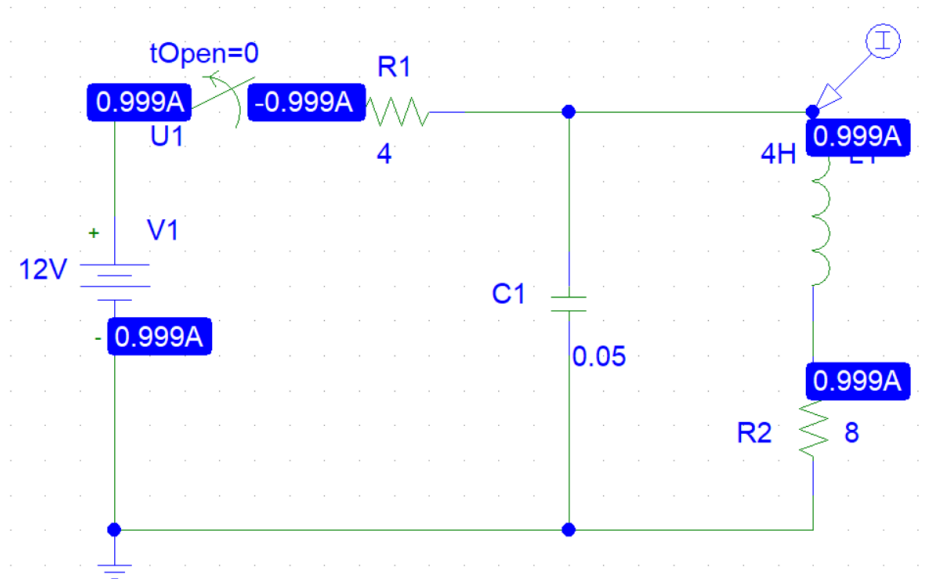


Fig.3.1.2

- Using Pspice, determine: the voltage $v_o(t)$ for the circuit in fig.3.2

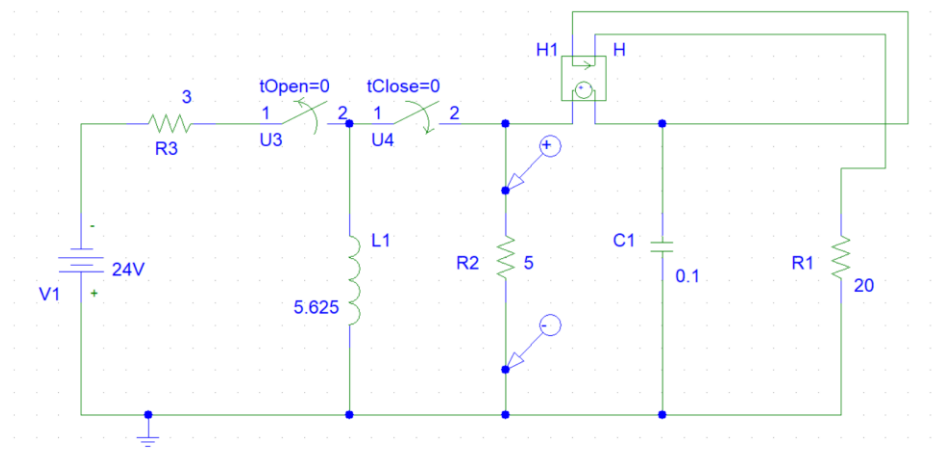


Fig.3.2.1

To get v_0 at R2:

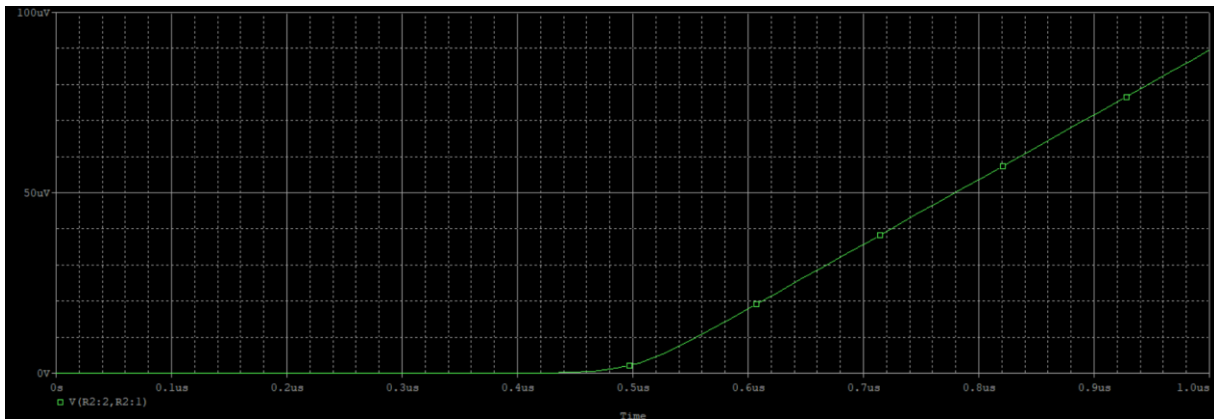


Fig.3.2.2

Question 5:

- Design a passive RC low pass filter with a cutoff frequency of 3000 Hz?

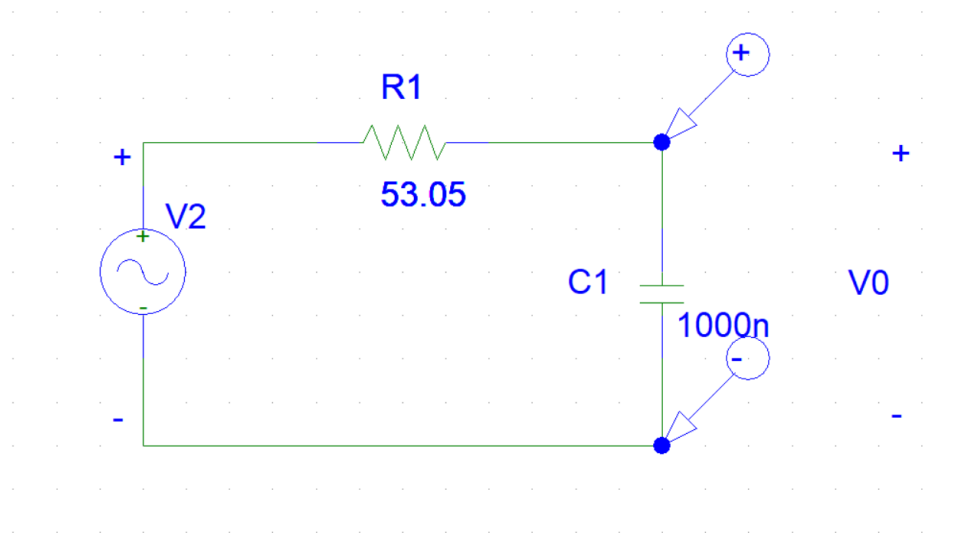


Fig.5.1

$F_c = 1/(2\pi RC)$, $f_c = 3000\text{Hz}$ and let $C = 1\mu\text{F}$

Therefore $R = 1/(2\pi C F_c) = 1/(2\pi(1\mu)(3000)) = 53.05\Omega$

- A bandpass filter has resonant frequency of 40krad/s and a quality factor of 5. Find the bandwidth, the upper cutoff frequency, and the lower cutoff frequency. Express all answers in kilohertz.

$\omega_0 = 40,000$, then $f_0 = 6366.2\text{Hz}$

$Q = 5$,

Then: $B=f_0/Q=1273.238\text{Hz}$

Finding upper cutoff frequency:

$F_h=f_0+B/2=7002\text{Hz}$

Finding lower cutoff frequency:

$F_l=f_0-B/2=5279.7\text{Hz}$

To find L, let $C=1\text{F}$ ----> $f_0=1/(2\pi*\text{sqrt}(LC))$

We get $L=6.25\text{ H}$

And $Q=(2\pi f_0 L)/R$ ----> $R=5\text{k}\Omega$

The circuit will be:

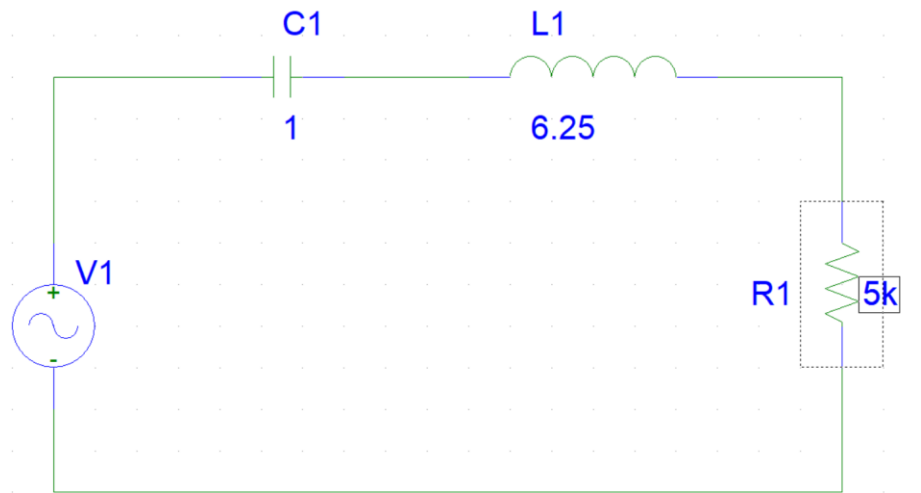


Fig5.2

Question 6:

The circuit shown in Figure below has two inputs, $v_s(t)$ and $i_s(t)$, and one output, $v(t)$. When inputs are

given by $V_s(t)=V_m \sin 6t\text{ V}$ and $i_s(t)=I_m\text{ A}$

the output will be

$v_o(t)=A \sin(6t+\alpha) + B\text{ V}$

Linearity requires that A be proportional to V_m and that B be proportional to I_m . Consequently, we can

write $A=k_1.V_m$ and $B=k_2.I_m$, where k_1 and k_2 are constants yet to be determined.

(a) Use PSpice to determine the value of k_1 by simulating the circuit, using $V_m=1\text{ V}$ and $I_m=0$.

Ans:

After building the circuit and put $V_m=1$ and $I_m=0$ as shown in fig6.1

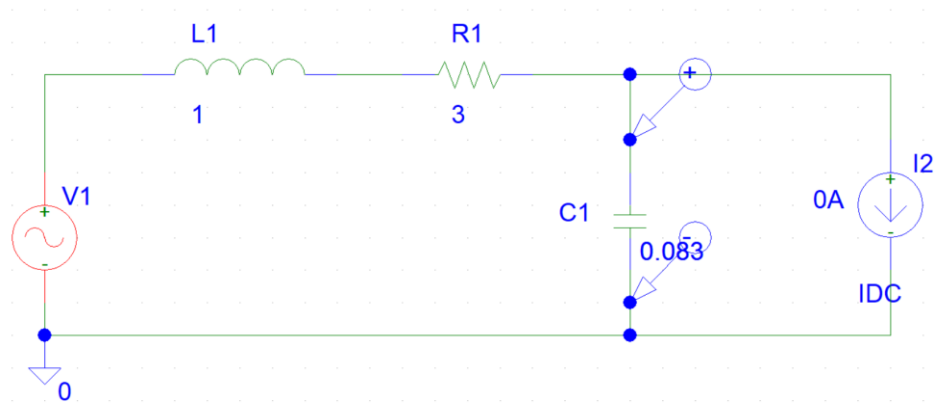


Fig6.1

After simulating the circuit as shown in the figure 6.1.1:

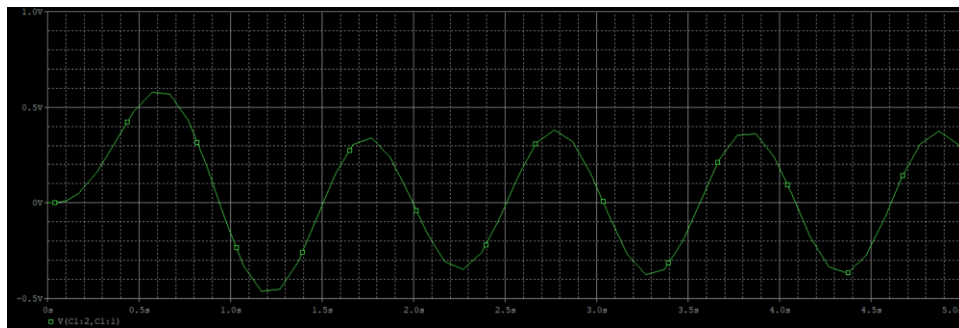


Fig6.1.1

We can see that the peak=0.405v

So $K_1=0.405/1=0.405$

(b) Use PSpice to determine the value of k_2 by simulating the circuit, using $V_m=0$ V and $I_m=1$.

After building the circuit and put $V_m=0$ and $I_m=1$ as shown in the fig6.2:

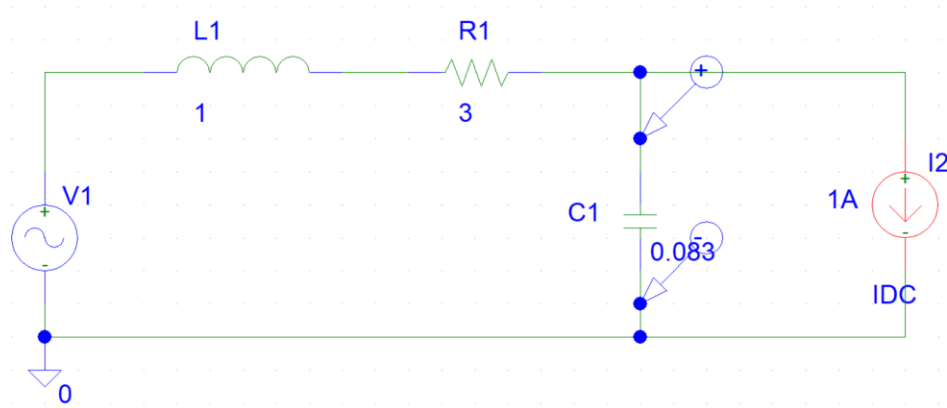


Fig6.2

After simulating the circuit as shown in fig6.2.1:

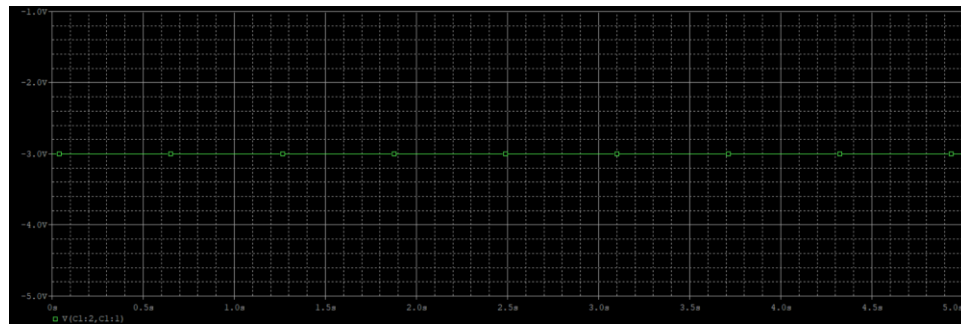


Fig6.2.1

We can see that the peak = -3

So $K_2 = -3/1 = -3$

(c) Knowing k_1 and k_2 , specify the values of V_m and I_m that are required to cause $v_o(t) = 5 \sin(6t + \alpha) + 5$

As we got: $k_1 = 0.405$ and $k_2 = -3$

$A = 0.405 \cdot V_m = 5$ so $V_m = 12.35 \text{ V}$

And $B = (-3)I_m = 5$ so $I_m = -1.67 \text{ V}$

$I_s = (-1.67) \cdot 5 = -8.35 \text{ A}$

V . Simulate the circuit, using PSpice to verify the specified values of V_m and I_m .

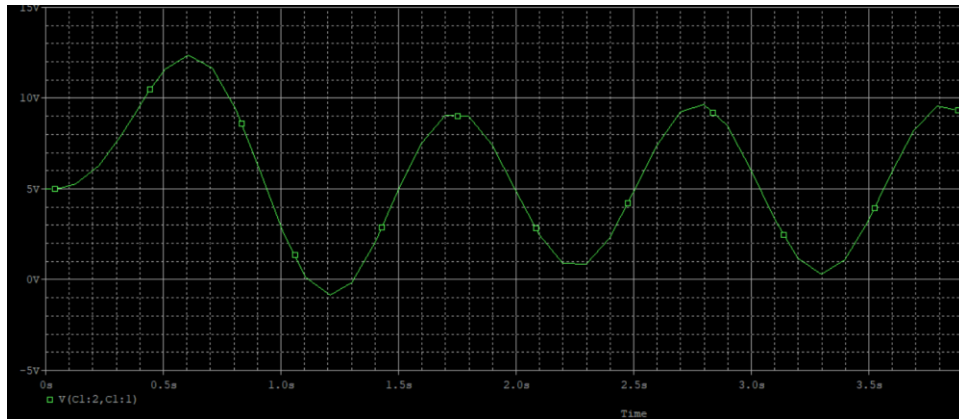


Fig6.3

(d) Determine the average power delivered by $v_s(t)$ using Pspice.

After putting voltage differential markers at $V_s(t)$ and simulating it :

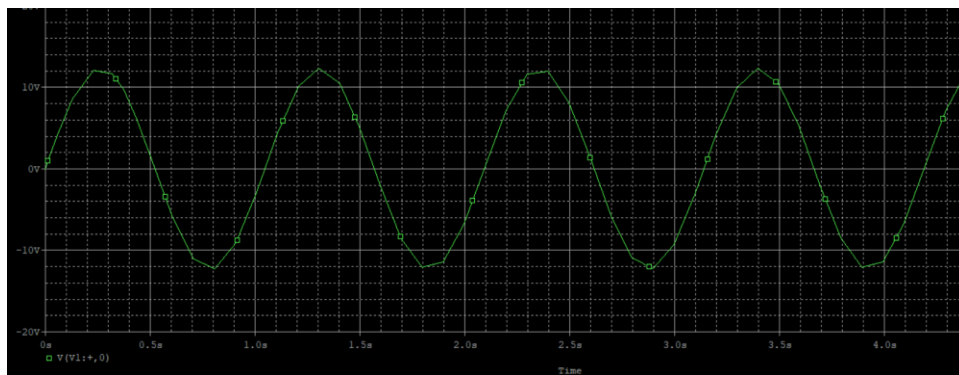


Fig6.4